 


**Question 1 [5 marks]** Given the truth table below, draw the minimum cost logic circuit where you can only use two-input NAND gates, two-input AND gates, and two-input OR gates. The inputs are only A, B and C while the output is Y.

Inputs			Output
A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1



**Question 2 [5 marks]** For the Karnaugh map given below, determine the minimum cost Sum-of-Products (SOP) expression. Inverted signals have a cost.

		$x_1 \ x_2$					
$x_3$	$x_4$			0 0	0 1	1 1	1 0
		0	1				
0	0			1	0	0	0
0	1			1	1	0	0
1	1			0	1	1	0
1	0			0	0	0	0


$$f = \bar{x}_1 \bar{x}_2 \bar{x}_3 + x_2 x_3 x_4 + \bar{x}_1 x_2 x_4$$

**Question 3 [5 marks]** Determine the minimum cost **Product of Sums (POS)** expression using the Karnaugh Map below. Inverted signals have a cost and d is don't-care.


$x_3 \backslash x_4$		$x_1 \ x_2$			
		0 0	0 1	1 1	1 0
0	0	1	1	d	0
0	1	d	d	0	d
1	1	0	1	1	0
1	0	d	1	0	0

$$f = (\overline{x_3} + x_2)(x_3 + \overline{x_1})(x_4 + \overline{x_1})$$

 **Question 4 [10 marks]** Replace the logic circuit given below with its minimum cost logic circuit. Inverters have a cost.



NAND gate can be used as well

 

Additional space on the next page

**Question 5 [15 marks total]** Using basic gates (AND, OR, NOT, NAND, NOR, XOR, XNOR) and flip-flops and latches, draw the circuit for each of the following portions of Verilog code.

a) (2 marks)

```
module test (a, b, f);
```


```
  input [1:0] a;
```

```
  input [1:0] b;
```

```
  output [1:0] f;
```

```
  assign f = a+b;
```

```
endmodule
```

 

b) (2 marks)

```
module test2 (clock, s, r, f);
```

```
  input clock, s, r;
```

```
  output reg f;
```


```
  always@(posedge clock)
```

```
  begin
```

```
    f <= s^r;
```

```
  end
```

```
endmodule
```

 

c) (4 marks)

```
module test3 (clock, s, r, resetn, f);
```

```
  input clock, s, r, resetn;
```

```
  output reg f;
```

```
  always@(*)
```

```
  begin
```

```
    if (clock == 1'b0)
```

```
      if (~resetn)
```


```
        f = s & r;
```

```
      else
```

```
        f = s | r;
```

```
    end
```

```
  endmodule
```

 

d) ( 7 marks)

```
module test4 (clock, w, z, resetn);
```

```
input clock, w, resetn;
```

```
output reg z;
```

```
reg [1:0] ps;
```

```
reg [1:0] ns;
```

```
always@(*)
```

```
case(ps)
```

```
2'b00: ns = 2'b01;
```

```
2'b01: if (w) ns = 2'b10; else ns = 2'b10;
```

```
2'b10: if (w) ns = 2'b11;
```

```
2'b11: if (w) ns = 2'b00; else ns = 2'b01;
```

```
endcase
```

```
always@(posedge clock or negedge resetn)
```


```
if (~resetn) ps <= 2'b00; else ps <= ns;
```

```
always@(*)
```

```
if (w) z = (ps == 2'b11);
```

```
else z = (ps == 2'b01);
```

```
endmodule
```

 

Additional space on next page

**Question 6 [10 marks total]** Suppose you have a system which in each clock period produces a signal 'w' that is set to 0 or 1. The system produces useful output in batches. A batch begins with a pair of 1s (i.e. 11) on the output 'w'. After the pair of 1s, the system sends a 3-bit message, which is only valid if the message represents an odd 3-bit number. An example of an arbitrary batch is: 11011. An example of an arbitrary pair of batches is: 1101111010.

Design a Finite State Machine (FSM) with minimal number of states that takes 'w' as input and produces two outputs; 'r' and 'v'. Output 'r' is asserted for one clock period once a complete batch has been detected and output 'v' is asserted at the same time if the message is valid.

Answer the following questions:

- (2 marks) Write a state table to describe your state machine.
- (2 marks) Create a state-assigned table for your FSM, using as few bits as possible for your state encoding.
- (4 marks) Show logic expressions for your next-state logic and your outputs.

a)

PS	NS		r v	
	w=0	w=1	<del>r</del>	v
A	A	B	0	0
B	A	C	0	0
C	D	<del>D</del>	0	0
D	E	E	0	0
E	F	G	0	0
F	A	B	1	0
G	A	B	1	1



Additional space for question 6

b)

PS ( $y_3 y_2 y_1$ )	NS ( $Y_3 Y_2 Y_1$ )		$z$ $v$	
	$w=0$	$w=1$		
000	000	001	0	0
001	000	010	0	0
010	011	011	0	0
011	100	100	0	0
100	101	110	0	0
101	000	001	1	0
110	000	001	1	1

c)

$Y_3$

$w y_3$ $y_2 y_1$	00	01	11	10
00		1	1	0
01				0
11	1	d	d	1
10				

$$Y_3 = \bar{y}_2 \bar{y}_1 y_3 + y_2 y_1$$

$Y_2$

$w y_3$ $y_2 y_1$	00	01	11	10
00			1	
01				1
11		d	d	
10	1			1

$$Y_2 = w y_3 \bar{y}_2 \bar{y}_1 + w \bar{y}_3 \bar{y}_2 y_1 + \bar{w} \bar{y}_3 y_2 \bar{y}_1 + w \bar{y}_3 y_2 \bar{y}_1$$

$Y_1$

$w y_3$ $y_2 y_1$	00	01	11	10
00		1		1
01			1	
11		d	d	
10	1		1	1

$$Y_1 = \bar{w} \bar{y}_3 \bar{y}_2 \bar{y}_1 + w \bar{y}_3 \bar{y}_2 \bar{y}_1 + w y_3 y_1 + w y_3 y_2 + \bar{y}_3 y_2 \bar{y}_1$$

$$z = y_3 y_2 + y_3 y_1$$

$$v = y_3 y_2$$